

Assignment -1

Academic Year 2024-25

Course Code: **2413FEE1T2**

Course Name: **BEE**





Date of Assignment: **24/09/2025**

Date of Submission: **06/10/2025**

CO1 and CO6

All questions compulsory (5M)

| | |
|----|---------------------------------------------------------------------------------------------------------------------------------|
| 1. | <p>Evaluate the current through the 3Ω resistor in the network shown in figure below using node analysis.</p> |
| 2. | <p>Find an equivalent resistance between terminals A and B.</p> |
| 3. | <p>Find an equivalent resistance between terminals A and B.</p> |
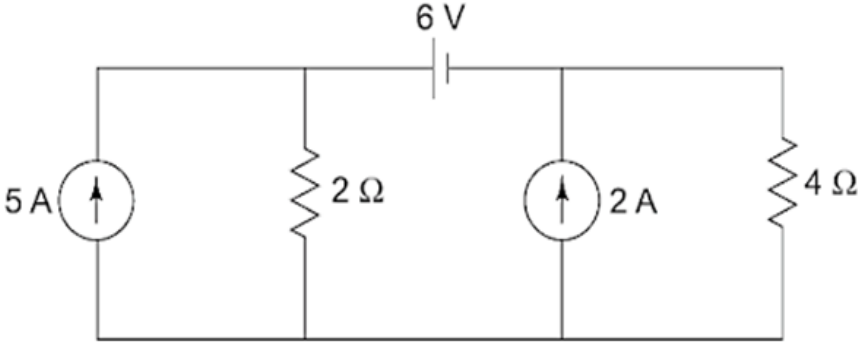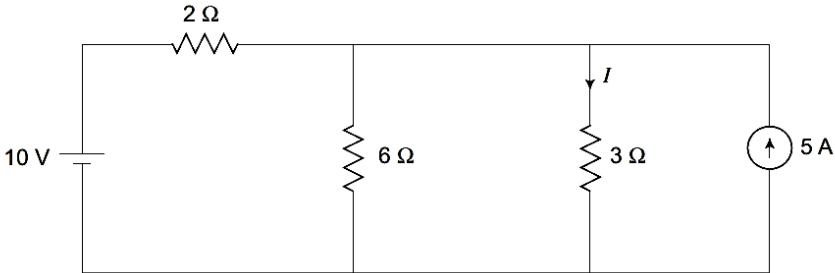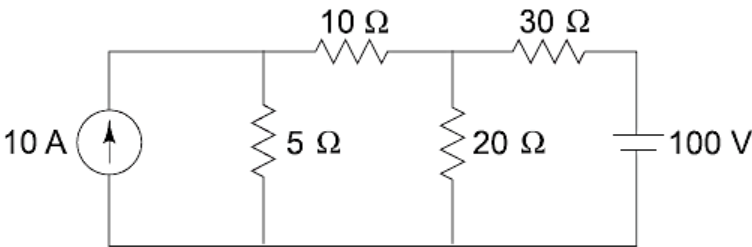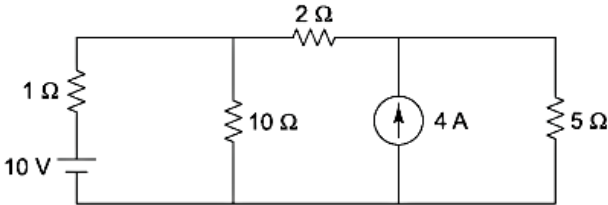
| | |
|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 4. | Find the value of current flowing in the $4\ \Omega$ resistor using source transformation.  |
| 5. | Find the value of current flowing through $3\ \Omega$ resistor using source transformation.  |
| 6. | Find the value of current flowing through the $10\ \Omega$ resistor using Thevenin's Theorem  |
| 7. | Using Superposition Theorem, find the values of current flowing in the $10\ \Omega$ resistor.  |
| 8. | Evaluate the current flowing through the $5\ \Omega$ resistor using Superposition Theorem |

| | |
|-----|-----------------------------------------------------------------------------------------------------------------------------------------|
| | |
| 9. | <p>Evaluate the current through the 3Ω resistor in the network shown in figure below using node analysis.</p> |
| 10. | <p>Using Node Analysis, find V_A and V_B</p> |
| 11. | <p>Evaluate the current flowing through the 2Ω resistor in the network shown in figure below using node analysis.</p> |
| 12. | <p>Find the value of current flowing through the 4Ω resistor using mesh analysis.</p> |

| | |
|-----|-------------------------------------------------------------------------------------------------------------------------------|
| 13. | <p>Evaluate the current flowing through the 2Ω resistor in the network shown below using mesh analysis.</p> |
| 14. | <p>Using Mesh analysis: find the values of current supplied by the battery.</p> |
| 15. | Explain different types of cables used for electrical installation. |
| 16. | What is the purpose of earthing in electrical installation? Explain different types of electrical earthing. |
| 17. | Give the difference between MCB and MCCB. |
| 18. | Write short note on Switchgears |